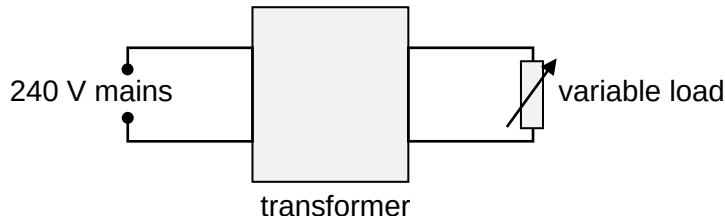


- 27 An ideal transformer steps down the 240 V sinusoidal voltage from the mains to 12 V, which is then applied to a variable load.



What is the change in the current supplied by the mains when the resistance of the load is increased from $20\ \Omega$ to $50\ \Omega$?

- A Decrease from 30 mA to 12 mA.
- B Increase from 12 mA to 30 mA.
- C Decrease from 12 mA to 4.8 mA.
- D Increase from 0.24 A to 0.60 A.

Ans: A

$$I_P / I_S = n_S / n_P = V_S / V_P = 12 / 240 = 0.050$$

$$\text{At } 20\ \Omega, I_S = 12 / 20 = 0.60\ \text{A} \rightarrow I_P = 0.60 \times 0.050 = 0.030\ \text{A}$$

$$\text{At } 50\ \Omega, I_S = 12 / 50 = 0.24\ \text{A} \rightarrow I_P = 0.24 \times 0.050 = 0.012\ \text{A}$$

- 28 The diagram shows two spectra of X rays from an X ray tube