

22	C	$I_T = I_1 + I_2$ $\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2}$ $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$ Since the resistors are in parallel, the p.d. across each resistor is the same.
23	C	$V = R \cdot I$