

		Since the resistors are in parallel, the p.d. across each resistor is the same.
23	C	$V_X = R_X I$ The graph for X is a straight line with positive gradient and it passes through the origin. $V_Y = E - R_X I$ The graph for Y is a straight line with negative gradient and positive vertical intercept, E . The current through the 2 resistors is always the same at any time. The total p.d. across the 2 resistors is always E . Hence as the reading of Y decreases, the reading of X increases.
24	D	