

		D = 3.00 m
18	B	Current in circuit, $I = \frac{V}{R} = \frac{10}{4.0} = 2.5 \text{ A}$, Potential difference across connecting wires $= 12 - 10.0 - (2.5)(0.20)$ $= 1.5 \text{ V}$ Power loss in connecting wires $= (2.5)(1.5)$ $= 3.75 \text{ W}$

10	A	5
----	---	---