

20	B	Electric potential decreases along the direction of electric field strength.
21.	D	By conservation of charges, $I_1 = I_2 + I_3$ ---- (1) Also for the parallel circuit, we note that $\frac{I_2}{I_3} = \frac{R_3}{R_2}$ ----- (2) Using (1) and (2) to eliminate I_2, (1) becomes $I_1 = I_3 \left(\frac{R_3}{R_2} \right) + I_3$, or $I_1 = I_3 \left(\frac{R_3}{R_2} + 1 \right)$, giving $\frac{I_3}{I_1} = \frac{R_2}{R_2 + R_3}$
22	C	