

20 Ans: B

From graph, when current is 40 mA, p.d. is approximately 1.2 V.

Therefore, p.d. across resistor = $6.0 - 1.2 = 4.8 \text{ V}$

$$R = V/I = (4.8)/(0.040) = 120 \text{ } \Omega$$

21 Ans: C