

22.

Ans: A

$$V_{R_1} = \frac{0.6}{1.0} V_{p.wire}$$

$$V_{R_2} = \frac{0.2}{1.0} V_{p.wire}$$

$$\frac{V_{R_2}}{V_{R_1}} = \frac{IR_2}{IR_1} = \frac{\frac{0.2}{1.0} V_{p.wire}}{\frac{0.6}{1.0} V_{p.wire}}$$

$$\frac{R_2}{R_1} = 0.33$$

23.

Ans: A