

19. Ans B

With another identical lamp added parallel to X, the effective resistance across X is halved of its initial value. Total resistance in the circuit drops. By potential divider principle, potential difference across X is smaller and across Y is larger. Brightness of the lamp depends on the power ($P=V^2/R$) delivered to lamp, hence X is less bright and Y is brighter.

