

$$\mathbf{8(a)(i)} \text{ Resistance } R = \frac{\rho l}{A} = \frac{(1.2 \times 10^{-5})(0.72)}{\pi(6.0 \times 10^{-2} \times 10^{-3})^2}$$

$$= 764 \, \Omega$$

$$\mathbf{(ii)} \text{ Power } P = \frac{V^2}{R} = \frac{230^2}{764} \text{ [1]}$$

$$= 69.2 \text{ W}$$


(iii) Material from filament will vaporise at high temperature.

(iv) 1. As filament gets thinner, its cross sectional area becomes effectively smaller [APPLICATION].

Since resistance $\propto 1/\text{cross sectional area}$ [CONCEPT], resistance increases [CONCLUSION].

2. Power output is inversely proportional to resistance ($P = \frac{V^2}{R}$) [CONCEPT]. Since resistance of bulb increases [APPLICATION], power will drop as voltage V is constant [CONCLUSION].

(v)

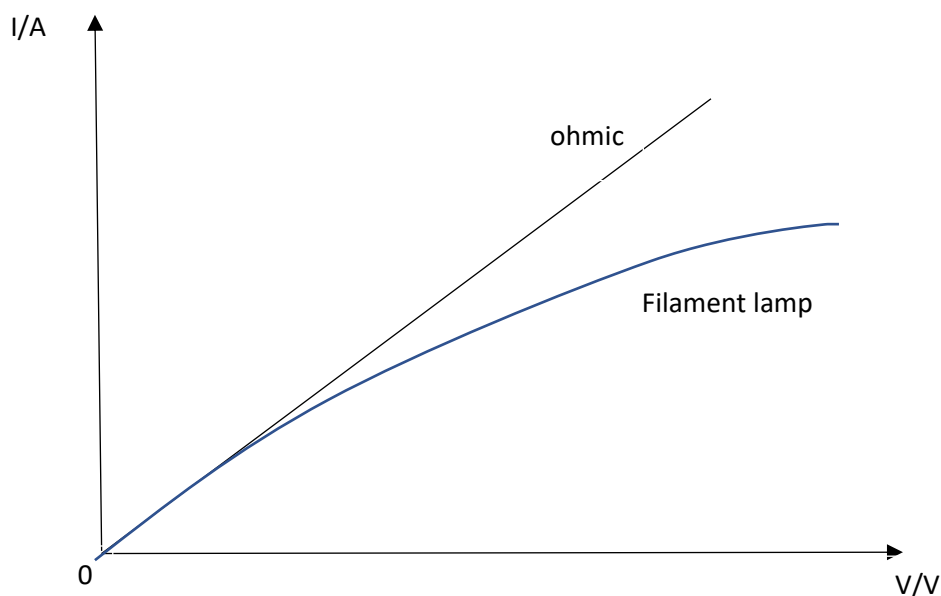

(b) (i) 1. 2.10 V

2. $W = QV = (1) (2.10) = 2.10 \text{ J}$

3. No current flows when switch is open and voltmeter is ideal.

No energy is being generated.

(ii) p.d. across internal resistor = $E - V = 2.10 - 2.00 = 0.10 \text{ V}$

By potential divider principle [CONCEPT],

Voltage across internal resistor = $\frac{r}{r+R} E$

$$0.10 = \frac{r}{r+10} (2.10)$$

$$r = 0.50 \Omega$$

(iii) Efficiency = $\frac{I^2 R}{I^2 (R+r)} = \frac{R}{R+r} = \frac{1}{1+\frac{r}{R}}$ [CONCEPT]

As R increases, $1 + \frac{r}{R}$ decreases [APPLICATION], hence efficiency increases [CONCLUSION].