

		$R_{rheostat} = 15.7 \approx 16 \Omega$
24	C	Given that the ammeter reading is zero, the p.d. across the 100Ω is the same as the p.d. across the 200Ω, i.e. $V_{100 \Omega} = V_{200 \Omega}$ Using potential divider, $\frac{100}{100 + 50} \times 12 = \frac{200}{200 + R} \times 24$ $R = 400 \Omega$

25	D	D = 1
----	---	-------