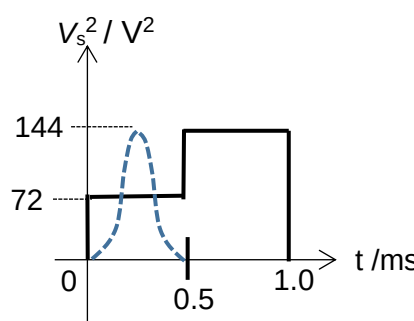
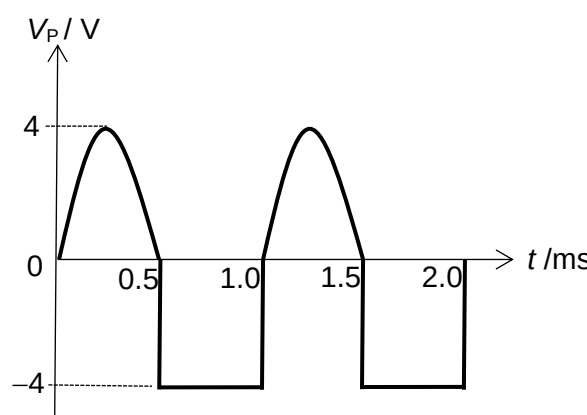


5	(a)	The value of voltage that is <u>equivalent to that of a steady d.c. voltage</u> which will dissipate energy <u>in a given resistor at the same rate.</u>	B1 B1				
	(b)(i)	Squaring the graphs and arranging the curved portion to a rectangle.  Mean-square-voltage = 108 V^2 Root-mean-square voltage = $10.39 \text{ V} = 10.4 \text{ V}$	M1 M1 A1				
	(b)(ii)	<table border="1"><tr><td>Diode 1</td><td>Forward-biased</td></tr><tr><td>Diode 2</td><td>Reverse-biased</td></tr></table> Both correct – [1] One or zero correct – [0]	Diode 1	Forward-biased	Diode 2	Reverse-biased	B1
Diode 1	Forward-biased						
Diode 2	Reverse-biased						
	(b)(iii)	Effective resistance across resistors P and Q = $10/2 = 5 \Omega$ Using potential divider rule, Max p.d. across P = $\frac{5}{10+5}(12) = 4.0 \text{ V}$	B1 B1				
	(b)(iv)	 Correct waveform (shape) for two cycles $-12 \text{ V} < V_p < 12 \text{ V}$ Numerical values of V_P not assessed	B1 B1				

6	(a)(i)	either wavelength is longer than threshold wavelength	
---	--------	---	--