

19. Ans: A

Explanation: Initially effective resistance is zero. As resistance of variable resistor is increased, the effective resistance increases until it is $R/2$. By potential divider rule, terminal p.d will increase.

20. Ans: B