

4 (a) (i) $V_{out} = 0.040 \times 80 = 3.2V$ [M1]
 potential at A = $0 - 3.2V = -3.2V$ [A1]

(ii) $V_x = 8.0 - 3.2 = 4.8V$ [C1]

$$R_x = \frac{4.8}{0.040} = 120\Omega$$
 [A1]

(b) (i) $R_{out} = \frac{100 \times 80}{100 + 80} = 44.44\Omega$ [C1]

$$V_{out} = \frac{R_{out}}{R_{total}} \times 8.0$$

$$= \frac{44.44}{44.44 + 120} \times 8.0$$
 [C1]

$$= 2.16 V$$
 [A1]

- (ii) When temperature gets hotter, resistance across the thermistor decreases [M1]

and hence effective/combined resistance across AB decreases. By applying potential divider rule, potential difference across BC increases [M1] which will turn on the fan.

Thus, fan should be connected across BC [A1]