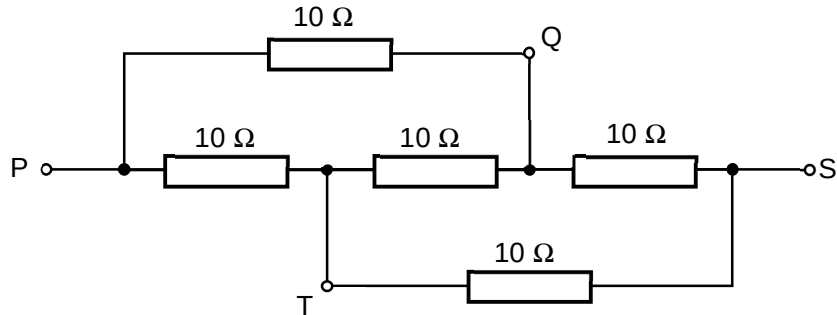


18 A network of resistors each of resistance $10\ \Omega$ are shown.



What is the effective resistance between Q and T?

- A** $2.0\ \Omega$
- B** $5.0\ \Omega$
- C** $10\ \Omega$
- D** $12\ \Omega$

19 The circuit diagram shows a battery of negligible internal resistance connected to three