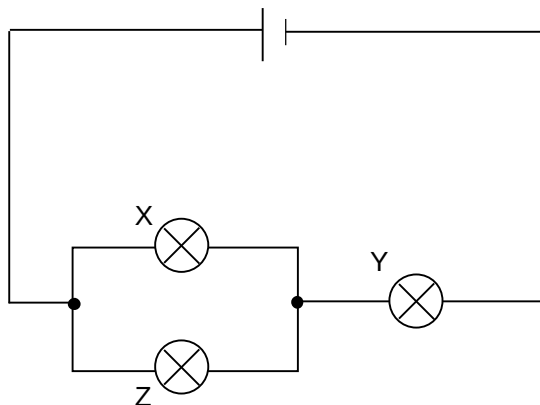


- 19** The circuit diagram shows a battery of negligible internal resistance connected to three identical bulbs X, Y and Z.



The filament of bulb X broke.

What happens to the brightness of bulb Y and bulb Z?

	bulb Y	bulb Z
A	brighter	dimmer
B	dimmer	brighter
C	remains the same	brighter
D	brighter	remains the same

20 In the diagram below, three identical bulbs are connected to form a circuit. The maximum