

Answer: B

- 19** Before X blows, p.d across X and Z < p.d. across Y.
After X blows, p.d across Z = p.d. across Y.
i.e., p.d. across Z increases and p.d. across Y decreases.

Hence Z's brightness increases and that of Y decreases.

Answer: B

20 Maximum power for circuit can be attained when the single bulb is at maximum power