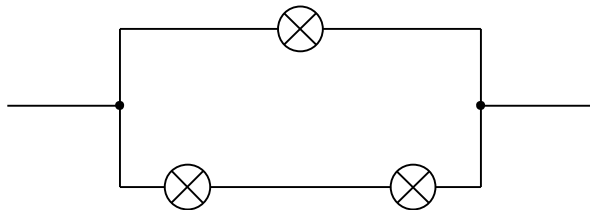


- 20** In the diagram below, three identical bulbs are connected to form a circuit. The maximum power produced by a single bulb is 10 W.



The resistance of the bulbs remains constant when lighted up.

What is the total maximum power that can be attained in this circuit such that all bulbs are lighted up?

A 10 W

B 15 W

C 20 W

D 30 W

- 21** Two long straight vertical wires run parallel to each other, carrying currents in opposite