

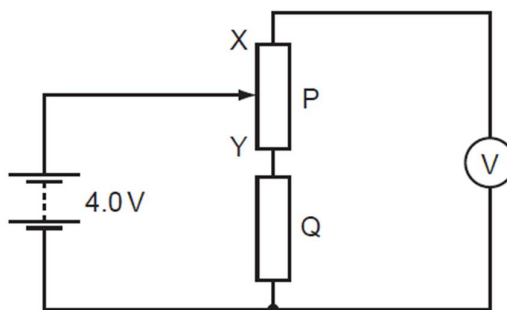
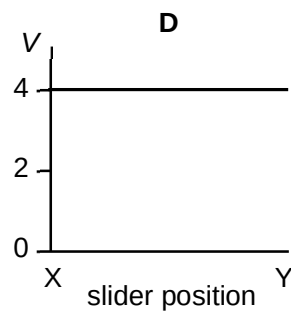
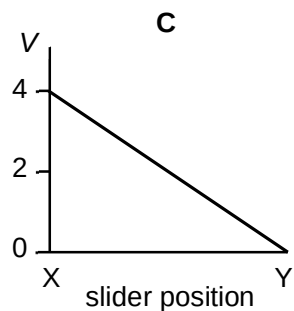


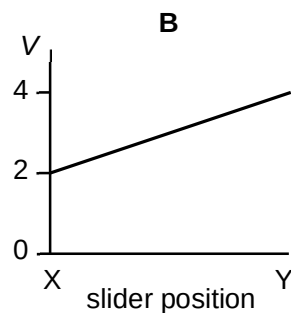- 21** In the circuit below, P is a potentiometer of total resistance $10\ \Omega$ and Q is a fixed resistor of resistance $10\ \Omega$. The battery has an e.m.f. of $4.0\ \text{V}$ and negligible internal resistance. The voltmeter has a very high resistance.



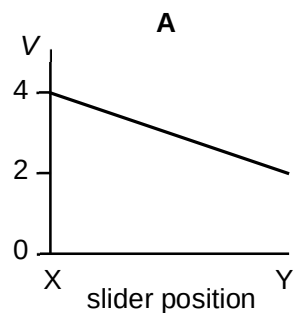What graph shows the variation with slider position of the voltmeter reading V as the slider on the potentiometer is moved from X to Y?



22 Eight resistors are arranged as shown