

Qn	Ans	Suggested Solution
21	D	Due to the high resistance of voltmeter, negligible current flows through it. Regardless of the slider position on the potentiometer P, the potential of the slider is always 4.0 V. Hence, the voltmeter is always measuring the e.m.f. of the battery.
22	A	Between X and Y the network is made of parallel resistors of resistance $70\ \Omega$.