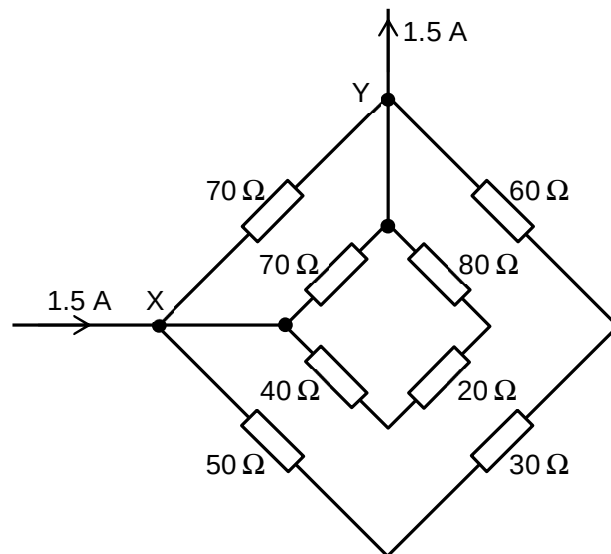


22 Eight resistors are arranged as shown.

A current of 1.5 A enters the network at junction X and leaves through junction Y.



What is the current in the resistor of resistance 30 Ω ?

- A** 0.25 A
- B** 0.50 A
- C** 0.75 A
- D** 1.0 A

23 Differently charged ions are all fired at the same speed into a region where there is a