

		the voltmeter is always measuring the e.m.f. of the battery.
22	A	Between X and Y, the network is made of parallel resistors of resistance $70\ \Omega$, $70\ \Omega$, $(40+20+80=140)\ \Omega$ and $(50+30+60=140)\ \Omega$. By proportionality, the $1.5\ \text{A}$ current is divided into 6 parts, i.e. $0.25\ \text{A}$. Current of $0.50\ \text{A}$ flows through each of the two $70\ \Omega$ resistors. Currents each of $0.25\ \text{A}$ flow through the $(40+20+80=140)\ \Omega$ and $(50+30+60=140)\ \Omega$. Resistors respectively. Hence, the current in $30\ \Omega$ resistor is $0.25\ \text{A}$.
23	B	The magnetic force provides the centripetal force necessary for the charge to move in a