

- 4 (a) Define *electromotive force* of a cell, and explain its difference from the *terminal potential difference* across the terminals of the cell.

.....

.....

.....

.....

.....

.....

..... [2]

- (b) The variation with current I of terminal potential difference V across a battery with e.m.f. E and internal resistance r is shown in Fig. 4.1.

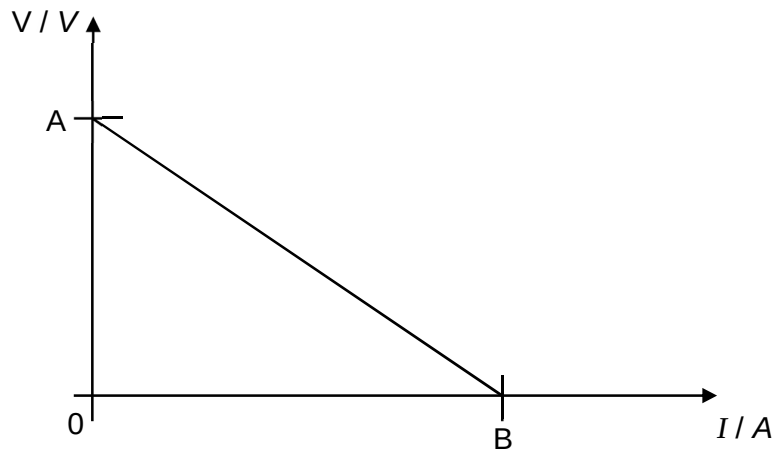


Fig. 4.1

In Fig. 4.1, state and explain the significance of the values of

- (i) the vertical intercept, A;

.....

.....

..... [2]

- (ii) the horizontal intercept, B.

.....

.....

.....

.....

..... [2]

