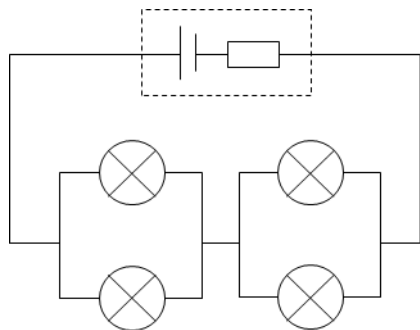



22 A battery with internal resistance is used to light up four identical bulbs.

Which of the following setup will have the highest efficiency?


A



B

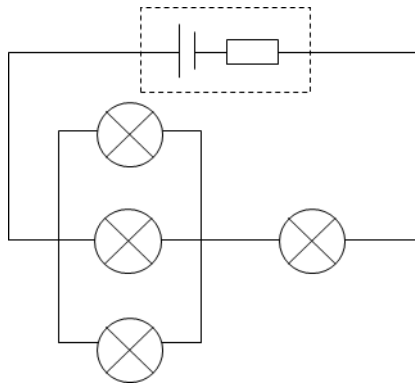

C

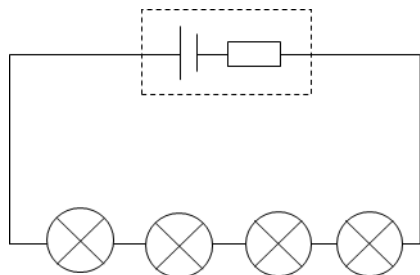

D

