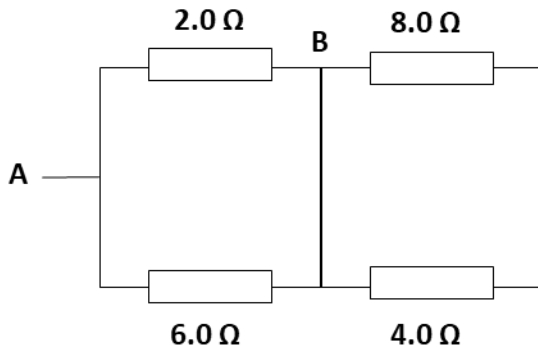


23 Four resistors are arranged in a setup as shown below.



What is the resistance across AB?

A $0.8\ \Omega$

B $1.5\ \Omega$

C $1.8\ \Omega$

D $4.2\ \Omega$