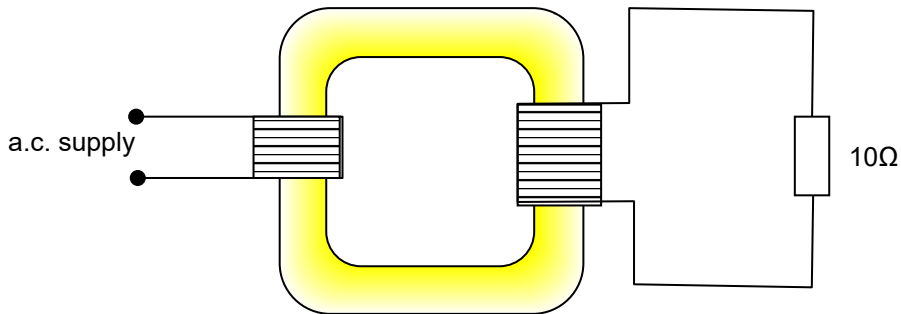


- 26** An ideal transformer has 100 primary turns and 500 secondary turns. A 20 V sinusoidal voltage is produced at the secondary when the load resistance is $10\ \Omega$.



The peak current in the primary coil is

- A** 2.0 A **B** 2.8 A **C** 10 A **D** 14 A

[Turn over]