

		$V_X > V_Z > V_Y$
23	C	When voltmeter connected, $I = \frac{5.0}{10} = 0.50 \text{ A}$ $E = 0.50 \times 30 = 15 \text{ V}$

		When ammeter is connected, R_2 will not have current passing through as ammeter has no resistance. Total resistance = $20\ \Omega$ $I = \frac{15}{20} = 0.75\text{ A}$