

23	D Effective resistance of the circuit increases when Bulb Q blows. Hence ammeter reading decreases. By PDP, the pd across P now decreases whereas pd across R increases, hence brightness of P decreases whereas R increases.
24	R