

	reading decreases. By $V = IR$, the pd across r now decreases whereas pd across R increases, hence brightness of P decreases whereas R increases.
24	B For maximum power to be delivered the value of the load resistor is equal to the internal resistance of the cell. i.e. $R = r = 2 \Omega$

	$I = \frac{E}{R+r} = \frac{10.0}{4} = 2.5 \text{ A}$ $P = (2.5)^2 \times 2 = 12.5 \text{ W}$
25	P