


27 A sinusoidal alternating current I / A varies with time t / s according to the equation

$$I = 2.0 \sin (100\pi t)$$


This current is allowed to pass through a resistor of resistance $5.0 \, \Omega$.

Which of the following shows how the power P / W dissipated in the resistor varies with t / s ?


A

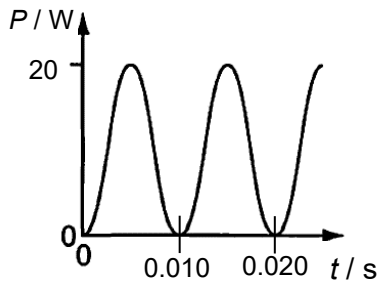


B

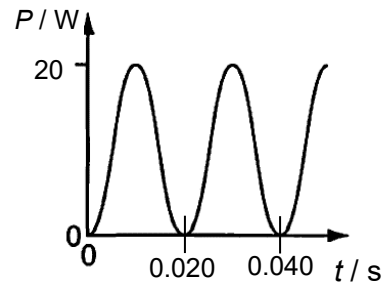

C

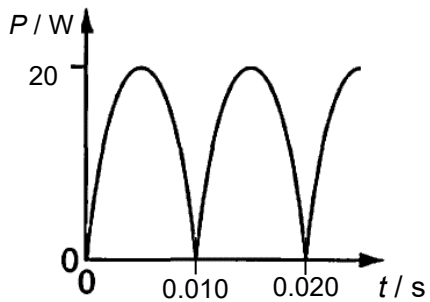

D

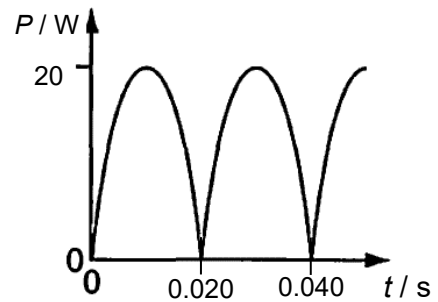

Answer: A

From the equation, compare with the general equation: $I = I_0 \sin (\omega t)$

$$I_0 = 2.0 \, \text{A} \quad \text{and} \quad \omega = 100\pi$$

$$P_0 = I_0^2 R = (2.0^2)(5.0) = 20 \, \text{W}$$

$$T = 2\pi/\omega = 2\pi/100\pi = 0.020 \, \text{s}$$

P-t graph is a sine-squared function.

28 The primary coil of an ideal transformer has 1000 turns and is connected to a sinusoidal