

21 by potential divider rule

$$\frac{3}{3 + 2 + R} = \frac{6 \times 10^{-3}}{2}$$

$$R = 995 \, \Omega$$