

so X is higher potential.

27 Eliminate A and B : $P = I^2 R$ so should be sine-squared instead of $|\sin|$

both resistors are in parallel so variation p.d. across R_2 is always same, which is that of source.

28 photoelectric effect: