

	has to be because the cross-sectional area is increasing.
22.	Ans: C p.d across load resistors: $\frac{1.5}{(2.0+1.5)} \times 9.0 = 3.857 \text{ V}$
23.	Ans: A