

21.

Answer: **B**

$$Q = It = \frac{V}{R} t$$

When all 3 switches are closed,

$$R_{\text{eff}} = \left(\frac{1}{4.0} + \frac{1}{6.0} \right)^{-1} = 2.4 \, \Omega \quad (\text{note that a short-})$$

$$Q_{\text{first minute}} = \frac{V}{R_{\text{eff}}} t = \frac{10}{2.4} (60)$$

When S2 and S3 are opened, $R_{\text{eff}} = 6.0 + 2.0 = 8.0 \, \Omega$

$$Q_{\text{second minute}} = \frac{V}{R_{\text{eff}}} t = \frac{10}{8.0} (60)$$

$$Q_{\text{total}} = \frac{10}{2.4} (60) + \frac{10}{8.0} (60) = 325 \, \text{C}$$