

22.	Answer: B Since the components are connected in series, the current is common and the potential difference across the components should add up to give 200 V. This occurs at $I = 0.30$ A. $V_x = 50$ V and $V_y = 150$ V $P_x = I_x V_x = 0.30 \times 50 = 15 \text{ W}$ $P_y = I_y V_y = 0.30 \times 150 = 45 \text{ W}$
23.	Answer: D