

	$P_y = I_y V_y = 0.30 \times 150 = 45 \text{ W}$
23.	Answer: D A and B are wrong because the diode is connected in reverse-bias. When temperature of the thermistor is low, resistance is high and hence p.d. across the thermistor is high. The heater should be connected across the thermistor.
24.	Ans: B Using right hand grip rule, the clockwise current in the coil generates a magnetic flux