

		vigorously vibration of lattice ions. The rate of collision between free electrons and lattice ions increases leading to increases in resistance.
21	B	Since the length of the wire is connected into the circuit, the current passing through the two cross-sections R and S is the same, i.e. the rate of flow of charge is the same.
22	A	The 3 Ω and 6 Ω resistors are connected in parallel while both the 2 Ω resistors are connected in parallel.