

		$v = 2.4 \times 10^4 \text{ m s}^{-1}$
23	A	COE: $E = IR + Ir$ $E = (3.0)(1.0) + (3.0)r \dots\dots\dots(1)$ $E = (2.0)(2.0) + (2.0)r \dots\dots\dots(2)$ Solving simultaneous equations: $E = 6.0 \text{ V}$
24	D	To shift the balance point to near Y, only increasing the resistance of the