
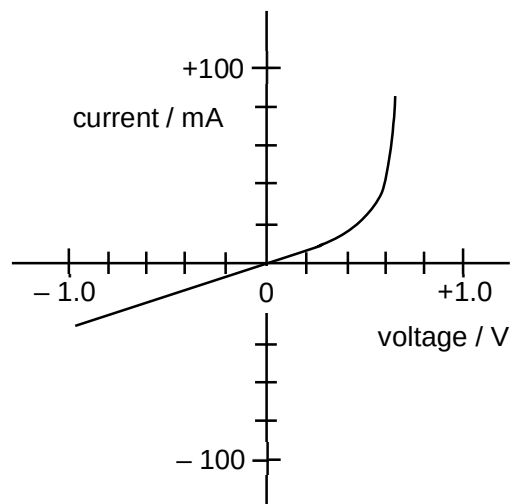


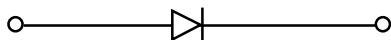- 20 A student is given a sealed box containing a concealed electrical circuit. The student plots the current-voltage characteristics below.




Which circuit is most likely to be enclosed within the box?

A




B

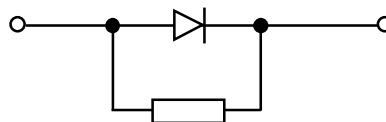

C



D

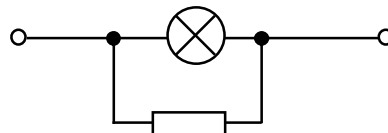

21 Four resistors are connected across a 10 V supply as shown in the circuit below