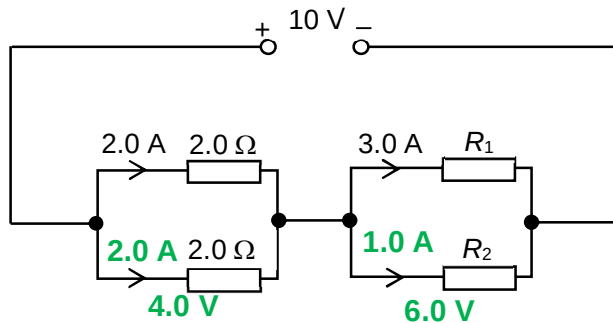


- 21 Four resistors are connected across a 10 V supply as shown in the circuit below.



What are the resistances R_1 and R_2 ?

	R_1	R_2
A	1.0Ω	3.0Ω
B	2.0Ω	2.0Ω
C	2.0Ω	6.0Ω
D	3.0Ω	3.0Ω

- 22 In the region of dimensions 10.0 cm by 1.00 m between two charged plates with a p.d. of