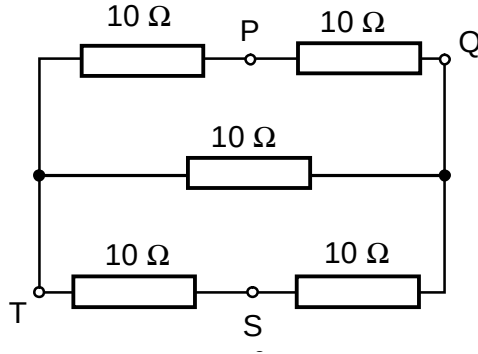


19 The given circuit is similar to the circuit below.



Thus, calculating the effective resistance across QT,

$$R_{QT} = \left(\frac{1}{10+10} + \frac{1}{10} + \frac{1}{10+10} \right)^{-1} = 5.0\ \Omega$$

Answer: B

20 When the resistance across the variable resistor increases the effective