

Answer: B

- 20** When the resistance across the variable resistor increases, the effective resistance across the variable resistor and the lamp increases. By potential divider rule, this will increase the p.d. across the lamp and the variable resistor. Thus, the brightness of the lamp increases, assuming the resistance of the lamp is constant.

Answer: B

- 21** By right hand grip rule magnetic flux density at O due to P and Q points in