

22	Answer: B At null point, $\frac{R}{2R} E_2 = \frac{3R}{3R + 2R + R} E_1$ Hence $\frac{E_1}{E_2} = 1.0$
23	Answer: A