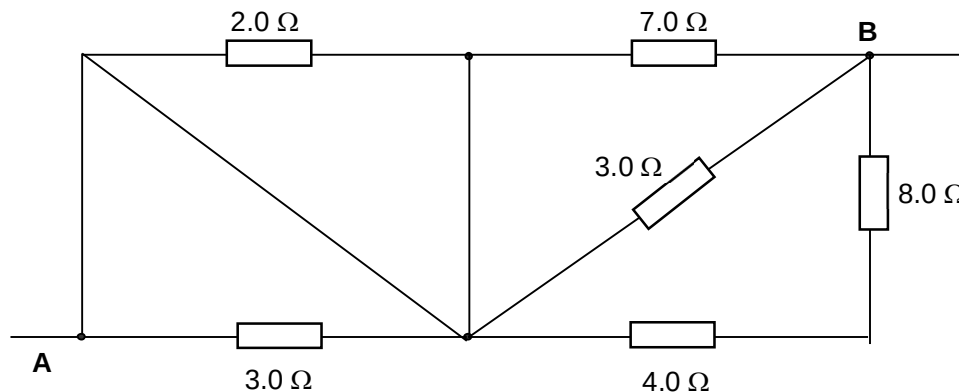


- 23 Six resistors are connected in a circuit as shown below.



What is the effective resistance of the circuit between terminals AB?

- A 1.2 Ω B 1.8 Ω C 3.0 Ω D 3.4 Ω

Ans: B

Distractors:

A: $7//3//8//4$

Options C and D both consider the 2.0 and 3.0 resistor.

C: $2//3 + 7//3//12$

D: $9 // [3 + 3// (8 \text{ and } 4)]$

24 The figure below shows the top view of a current balance where the rigid rectangular wire loop