

$$\frac{2A}{4} = \frac{A}{4}$$

19 C Energy = power x time = $VIt = VQ = 12 \times 4.0 = 48 \text{ J}$
 Current $I = Q/t$ so time $t = Q/I = 4.0/2.0 = 2.0 \text{ s}$

20 A Combined resistance of R_1 and $R_2 = R/2$