

Hence, R_1 has the greatest potential difference.

21 D By potential divider principle, voltmeter reading increases when effective resistance across thermistor is increased or resistance R_3 is reduced.

22 B $E_p - mg = ma$