

- 4 (a) p.d. across one lamp = 2.5 V C2
 resistance = $[(8.7 - 7.5) / 0.3] / 2$
 = 2.0 Ω A1
- (b) straight line through the origin M1
 with gradient of 0.5. A1
- (c) $P = I^2 R$
 = $0.30^2 \times 2.0$
 = 0.18 W A1
- Alternative method:
 use $P = V I$ or $P = V^2 / R$
- (d) (i) $R = \rho l / A$ C1
 $l = (2.0 \times 0.40 \times 10^{-6}) / 1.7 \times 10^{-8}$
 = 47 m A1
- (ii) $I = A n v q$
 $v = 0.30 / (0.40 \times 10^{-6} \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19})$ C1
 = $5.5 \times 10^{-5} \text{ m s}^{-1}$ A1

