

21 C

When a $500\ \Omega$ resistance is connected in parallel with the $1000\ \Omega$ R_2 , the effective resistance of these two resistors become smaller than $500\ \Omega$. Hence the p.d across R_2 will become smaller than before, while the p.d across R_1 will be larger than before.

22 A