

		$\pi \epsilon_0 l$
20	C	current across r is $\left(\frac{E}{2R + r}\right)$. Hence $P = \left(\frac{E}{2R + r}\right)^2 r$
21	A	$\frac{1}{2} \rho l = \frac{1}{2} \rho (3l)$