

23	D	At null deflection, no current flows through secondary cell, hence no effect if you placed resistor in series with it.
24	D	Using a resistor in series with the secondary cell will not affect the null deflection.