

22	C Option A: Resistance of thermistor increases. By potential divider, p.d across thermistor increases. Hence voltmeter reading is negative. Option B: By potential divider, p.d across fixed resistor will decrease. Voltmeter reading will be negative. Option C: Resistance of LDR increases. By potential divider, p.d across thermistor decreases. Hence voltmeter reading is positive. Option D: same effect as Option B.	D
23	C	D